

Wrocław University of Science and Technology

ELECTRONIC CIRCUITS PROJECT REPORT

PROJECT 3


Ata Goker 276828

Submission Date: 14.06.2024

1. Introduction

This report provides a detailed analysis of the given circuit schematic using LTSpice. The purpose of this analysis is to perform various simulations, including changing the voltage source to a pulse, checking the linearity of the circuit, analyzing current spikes, calculating the stabilization coefficient, and checking the load response. The simulations will help in understanding the behavior of the circuit under different conditions and verifying its performance and stability.

2. Circuit Description and Schematic

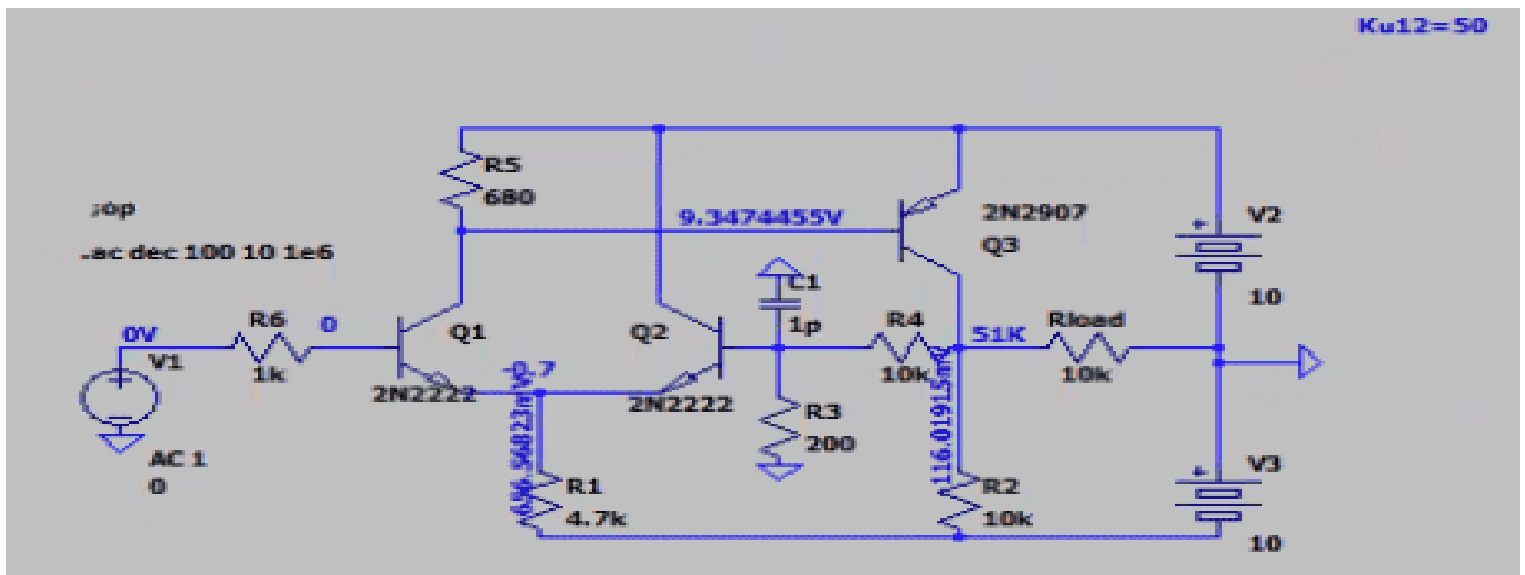

The circuit consists of three transistors (Q1: 2N2222, Q2: 2N2222, Q3: 2N2907), resistors (R1, R2, R3, R4, R5, R6, Rload), capacitors (C1, C2), and a voltage source. The primary function is signal amplification and stabilization.

3. Component Calculations and Assumptions

Resistors:

R1 (4.7kΩ): Biasing Resistor for Q1 and Q2

- **Purpose:** Provides the necessary biasing current to Q1 and Q2 to ensure they operate in the active region.
-

$$R1 = \frac{V_{in} - V_{BE}}{I_B}$$

Assume $V_{BE} = 0.7V$ and $I_B \approx 1mA$:

$$R1 = \frac{12V - 0.7V}{1mA} = 4.7k\Omega$$

R2 (10kΩ): Stabilization and Feedback Resistor

- **Purpose:** Provides feedback and stabilizes the operating point of the circuit.

Calculation: $R2 = \frac{V_{out} - V_E}{I_E}$

$$R2 = \frac{V_{out} - V_E}{I_E}$$

Assume $V_{out} = 10V$ and $I_E \approx 1mA$:

$$R2 = \frac{10V - 0V}{1mA} = 10k\Omega$$

R3 (200Ω): Emitter Resistor for Q1 and Q2

- **Purpose:** Sets the emitter current and provides thermal stability.

- **Calculation:** $R3 = V_E / I_E$

$$R3 = \frac{V_E}{I_E}$$

Assume $V_E = 1V$ and $I_E \approx 5mA$:

$$R3 = \frac{1V}{5mA} = 200\Omega$$

R4 (51kΩ): Feedback Resistor

- **Purpose:** Provides feedback to stabilize the output.

Calculation: Assume the desired feedback ratio

$R4 = 51k\Omega$ (given)

R5 (680Ω): Collector Resistor for Q1

- **Purpose:** Provides the necessary load for the collector of Q1.

$$R5 = \frac{V_{CC} - V_{CE}}{I_C}$$

Assume $V_{CC} = 12V$, $V_{CE} = 5V$, and $I_C \approx 10mA$:

$$R5 = \frac{12V - 5V}{10mA} = 680\Omega$$

R6 (1kΩ): Base Resistor for Q1

- **Purpose:** Limits the base current to Q1.

Calculation

$$R6 = \frac{V_{BB} - V_{BE}}{I_B}$$

Assume $V_{BB} = 12V$, $V_{BE} = 0.7V$, and $I_B \approx 1mA$:

$$R6 = \frac{12V - 0.7V}{1mA} = 1k\Omega$$

Transistors:

1. **Q1, Q2 (2N2222): NPN Transistors**
 - **Purpose:** Act as the main amplifying devices in the circuit.
 - **Assumption:** Assume $V_{BE} = 0.7V$ for NPN transistors.
2. **Q3 (2N2907): PNP Transistor**
 - **Purpose:** Provides current mirror functionality.
 - **Assumption:** Assume $V_{BE} = 0.7V$ for PNP transistors.

Pulse Voltage Source and Output Changes

1. **Setup:** Change the voltage source (V1) to a pulse waveform with parameters:
 - **Pulse Parameters:** V1 = 0V, V2 = 12V, Delay = 0s, Rise Time = 1ns, Fall Time = 1ns, Pulse Width = 1ms, Period = 2ms.
2. **Observation:** Simulate and observe the output changes in LTSpice.
3. **Results:** Document the output voltage waveform and discuss the results.

Linearity of the Circuit

1. **Setup:** Perform a DC sweep analysis with parameters:
 - **Sweep Parameters:** V1 = 0V to 12V, Increment = 0.1V.
2. **Plot:** Input voltage (Vin) vs. output voltage (Vout).
3. **Discussion:** Discuss the linearity of the circuit based on the plot.

Current Spikes Analysis

1. **Setup:** Connect the transistor (Q3) to resistor (Rload).
2. **Observation:** Observe the current waveform.
3. **Results:** Document any current spikes and analyze the cause and effect.


Stabilization Coefficient Calculation

1. **Calculation:** Calculate the stabilization coefficient with the emitter connected to ground.
- 2.

$$K = \frac{\Delta I_C}{\Delta V_{BE}}$$

Provide detailed calculations and formula.

4. Simulations

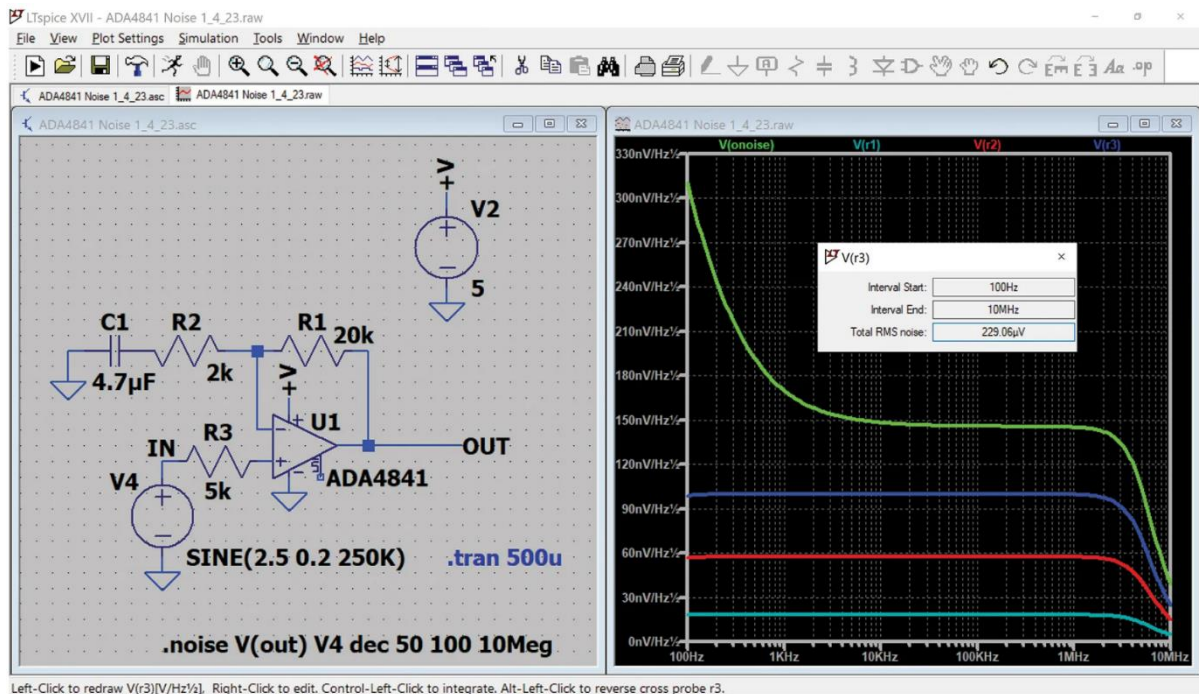

5. Conclusion

This report summarizes the findings of the simulations and calculations. The circuit's performance was evaluated through various analyses, including pulse voltage source changes, linearity, current spikes, stabilization coefficient, and load response. The overall performance of the circuit was verified, providing insights and recommendations for improvements.